

# CS 211: Computer Architecture

## Digital Logic

### Topics:

- Transistors
- Logic Gates
- Boolean algebra

# Transistor: Building Block of Computers

Microprocessors contain millions (billions) of transistors

- Intel Pentium 4 (2000): 48 million
- IBM PowerPC 750FX (2002): 38 million
- IBM/Apple PowerPC G5 (2003): 58 million

Logically, each transistor acts as a switch

Combined to implement logic functions


- AND, OR, NOT

Combined to build higher-level structures

- Adder, multiplexer, decoder, register, ...

Combined to build processor

# Simple Switch Circuit

 

Switch **open**:

- No current through circuit
- Light is **off**
- $V_{out}$  is **+2.9V**

Switch **closed**:

- Current flows
- Light is **on**
- $V_{out}$  is **0V**

**Switch-based circuits** can easily represent two states:  
on/off, open/closed, voltage/no voltage.


# n-type MOS Transistor

MOS = Metal Oxide Semiconductor

- two types: n-type and p-type

n-type

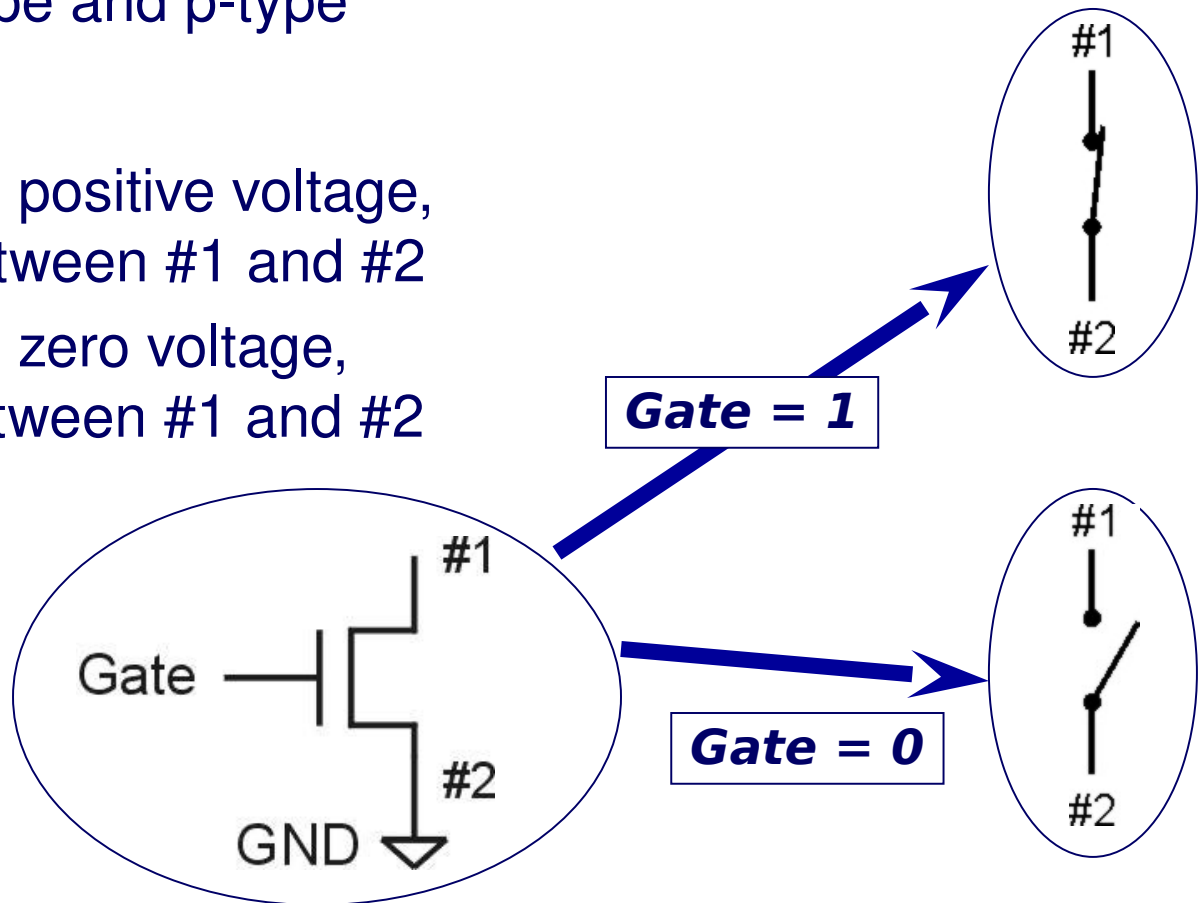
- when Gate has positive voltage, short circuit between #1 and #2
- when Gate has zero voltage, open circuit between #1 and #2


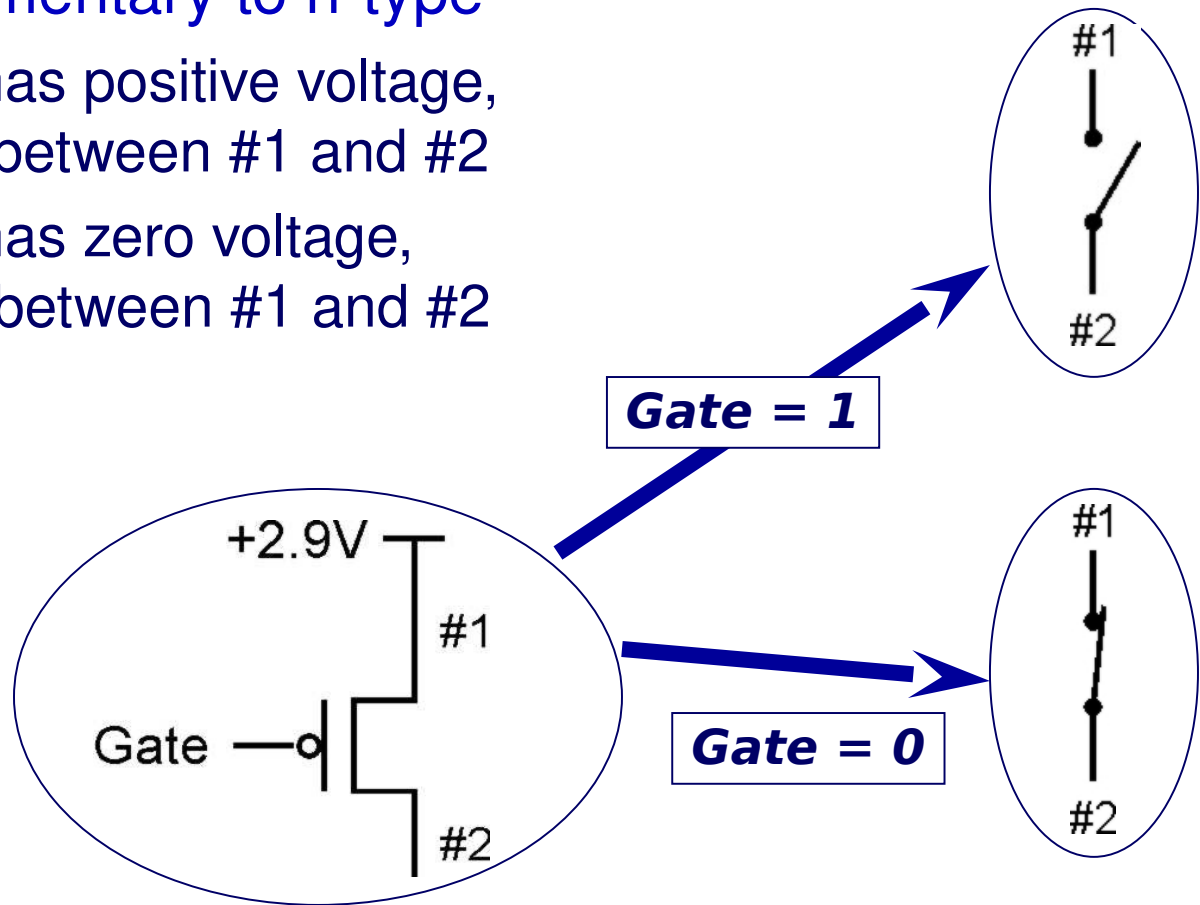
# p-type MOS Transistor

p-type is complementary to n-type

- when Gate has positive voltage, open circuit between #1 and #2
- when Gate has zero voltage, short circuit between #1 and #2




# Logic Gates

Use transistors to implement logical functions: AND, OR, NOT

Digital symbols:

 - recall that we assign a range of analog voltages to each digital (logic) symbol



- assignment of voltage ranges depends on electrical properties of transistors being used
  - typical values for "1": +5V, +3.3V, +2.9V
  - from now on we'll use +2.9V

# CMOS Circuit

## Complementary MOS



Uses both n-type and p-type MOS transistors

- p-type
  - Attached to + voltage
  - Pulls output voltage UP when input is zero
- n-type
  - Attached to GND
  - Pulls output voltage DOWN when input is one

MOS transistors are combined to form Logic Gates

For all inputs, make sure that output is either connected to GND or to +, but not both!


# Inverter (NOT Gate)

  

*Truth table*



In	Out
0 V	2.9 V
2.9 V	0 V

In	Out
0	1
1	0

 




# NOR Gate

  

A	B	C
0	0	1
0	1	0
1	0	0
1	1	0

**Note: Serial structure on top, parallel on bottom.**



# OR Gate

 

A	B	C
0	0	0
0	1	1
1	0	1
1	1	1

*Add inverter to NOR.*


# NAND Gate (AND-NOT)

  

A	B	C
0	0	1
0	1	1
1	0	1
1	1	0

**Note: Parallel structure on top, serial on bottom.**


# AND Gate

 

A	B	C
0	0	0
0	1	0
1	0	0
1	1	1


*Add inverter to NAND.*

# What is this?

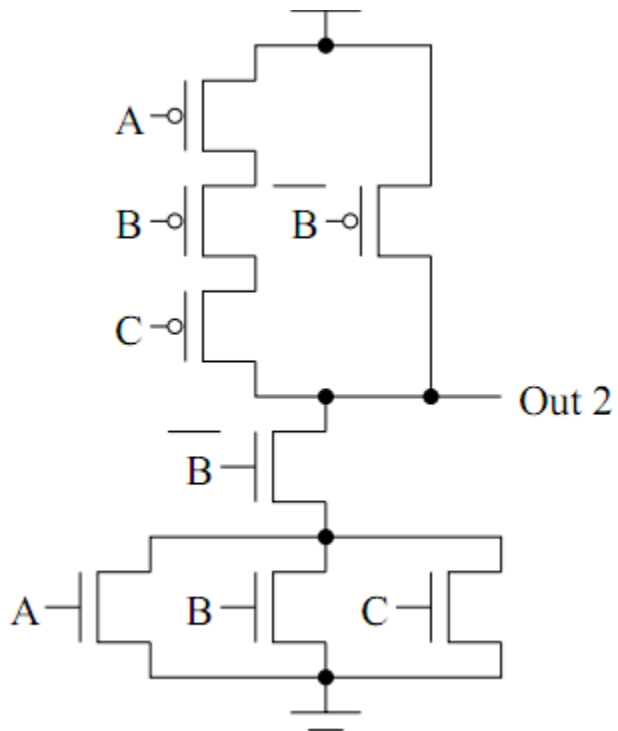


A	B	C	Out
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1


# Basic Logic Gates Symbols

 


*NOT*

 


*OR*

 

*NOR*

 

*AND*

 


*NAND*

# More than 2 Inputs?

AND/OR can take any number of inputs.

- $\text{AND} = 1$  if all inputs are 1.
- $\text{OR} = 1$  if any input is 1.
- Similar for NAND/NOR.

 
Can implement with multiple two-input gates.



# Logical Completeness

Can implement ANY truth table with AND, OR, NOT.

A	B	C	D
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	0

 

1. **AND combinations that yield a "1" in the truth table.**


2. **OR the results of the AND gates.**



# DeMorgan's Law

Converting AND to OR (with some help from NOT)

Consider the following gate:

 

A	B	$\overline{A}$	$\overline{B}$	$\overline{A} \cdot \overline{B}$	$\overline{\overline{A} \cdot \overline{B}}$
0	0	1	1	1	0
0	1	1	0	0	1
1	0	0	1	0	1
1	1	0	0	0	1

Same as  $A+B$ !

***To convert AND to OR  
(or vice versa),  
invert inputs and output.***

***Generally, DeMorgan's Laws:***

1.  $\overline{PQ} = \overline{P} + \overline{Q}$

2.  $\overline{P + Q} = \overline{P} \overline{Q}$

# NAND and NOR Functional Completeness

Any gate can be implemented using either NOR or NAND gates.

Why is this important?

- When building a chip, easier to build one with all of the same gates.

# NAND, NOR universality

NAND, NOR universal because they can realize AND, OR, NOT

$\bar{A} = A \text{ NAND } A$	$\bar{A} = A \text{ NOR } A$
$AB = \overline{A \text{ NAND } B}$	$A+B = \overline{A \text{ NOR } B}$
$A+B = \overline{A \text{ NAND } B}$	$AB = \overline{A \text{ NOR } B}$

# Terminology

Binary variable: a symbolic representation that might be 0 or 1 (eg. X, Y, A, B)

Complement: the opposite value of variable X

Literal: a boolean variable or its complement (eg, X,  $\overline{X}$ )

Expression: a set of literals combined with logical operations (eg.  $AB + C$ )

# Boolean algebra

- Values: 0, 1
- Operations: and, or, not, xor, implies, etc.
  - X AND Y: like multiplication
  - X XOR Y: like addition (mod 2)

	0	1
0	0	0
1	0	1

	0	1
0	0	1
1	1	0

# Boolean Identities

OR	AND	NOT	
$X+0 = X$	$X1 = X$		(identity)
$X+1 = 1$	$X0 = 0$		(null)
$X+X = X$	$XX = X$		(idempotent)
$X+\overline{X} = 1$	$X\overline{X} = 0$		(complementarity)
		$\overline{\overline{X}} = X$	(involution)
$X+Y = Y+X$	$XY = YX$		(commutativity)
$X+(Y+Z) = (X+Y)+Z$	$X(YZ) = (XY)Z$		(associativity)
$X(Y+Z) = XY + XZ$	$X+YZ = (X+Y)(X+Z)$		(distributive)
$\overline{\overline{X+Y}} = \overline{X} \overline{Y}$	$\overline{XY} = \overline{X} + \overline{Y}$		(DeMorgan's theorem)

# Boolean Algebra Example

$$F = \overline{X}YZ + \overline{X}Y\overline{Z} + XZ$$

$$\overline{X}Y(Z + \overline{Z}) + XZ \quad (\text{by reverse distribution})$$

$$\overline{X}Y1 + XZ \quad (\text{by complementarity})$$

$$\overline{X}Y + XZ \quad (\text{by identity})$$

# Boolean Algebra Example 2

Find the complement of F

$$F = A\bar{B} + \bar{A}B$$

$$\bar{F} = \overline{A\bar{B} + \bar{A}B}$$

$$(\overline{A\bar{B}})(\overline{\bar{A}B})$$

(by DeMorgan's)

$$(\bar{A} + B)(A + \bar{B})$$

(by DeMorgan's)

$$(\bar{A} + B)(A + \bar{B})$$

(by involution)



# Using DeMorgan's Laws to Complement

1. Big bar over AND and OR of 2 or more functions
2. Replace AND with OR, OR with AND
3. 1 with 0, 0 with 1
4. F with not(F), not(F) with F

$$\begin{aligned}& \overline{\overline{ABC} + \overline{ACD} + B\overline{C}} \\&= (\overline{ABC})(\overline{ACD})(\overline{B\overline{C}}) \\&= (\overline{ABC})(\overline{ACD})(B+C) \\&= \overline{ABC}D + \overline{ABC}\overline{D} \\&= \overline{ABC}D\end{aligned}$$

$$\begin{aligned}F &= \overline{ABC}, G = \overline{ACD}, H = B\overline{C}, \overline{F+G+H} = \overline{F}\overline{G}\overline{H} \\(\overline{ABC})(\overline{ACD}) &= \overline{ABC}D, F = B, G = \overline{C}, \overline{FG} = \overline{F} + \overline{G}\end{aligned}$$

# Duals


All boolean expressions have duals

Any theorem you prove, you can also prove for the dual

To form a dual

1. replace AND with OR, OR with AND
2. replace 1 with 0, 0 with 1

# Complements and Duals

 

# Complement Using Duals

Get dual and then complement each literal

$$F = X + A (Z + \bar{X} (Y + W) + \bar{Y} (Z + W))$$

$$\text{Dual: } F_{\text{dual}} = X (A + Z (\bar{X} + YW)(\bar{Y} + ZW))$$

$$\bar{F} = \bar{X} (\bar{A} + \bar{Z} (X + \bar{Y}\bar{W})(Y + \bar{Z}\bar{W}))$$

# Simplifying Expressions

