

CS 211: Computer Architecture

Digital Logic

Topics:

- Converting truth tables to expressions
- Karnaugh maps

Converting Truth Table to Boolean Expression

sensor
inputs

A	B	C	Output
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

Given a circuit, isolate the rows in which the output of the circuit should be **true**

Converting Truth Table to Boolean Expression

sensor inputs

A	B	C	Output
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

sensor inputs

A	B	C	Output
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

$\overline{A}BC = 1$
 $A\overline{B}C = 1$
 $AB\overline{C} = 1$
 $ABC = 1$

Given a circuit, isolate that rows in which the output of the circuit should be true

A product term that contains exactly one instance of every variable is called a minterm

Converting Truth Table to Boolean Expression

sensor
inputs

A	B	C	Output	
0	0	0	0	
0	0	1	0	
0	1	0	0	
0	1	1	1	$\bar{A}BC = 1$
1	0	0	0	
1	0	1	1	$A\bar{B}C = 1$
1	1	0	1	$AB\bar{C} = 1$
1	1	1	1	$ABC = 1$

$$\text{Output} = \bar{A}BC + A\bar{B}C + AB\bar{C} + ABC$$

Given the expressions for each row, build a larger Boolean expression for the entire table.

- This is a **sum-of-products (SOP)** form.


Converting Truth Table to Boolean Expression

sensor inputs

A	B	C	Output
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

$\bar{A}BC = 1$
 $A\bar{B}C = 1$
 $AB\bar{C} = 1$
 $ABC = 1$

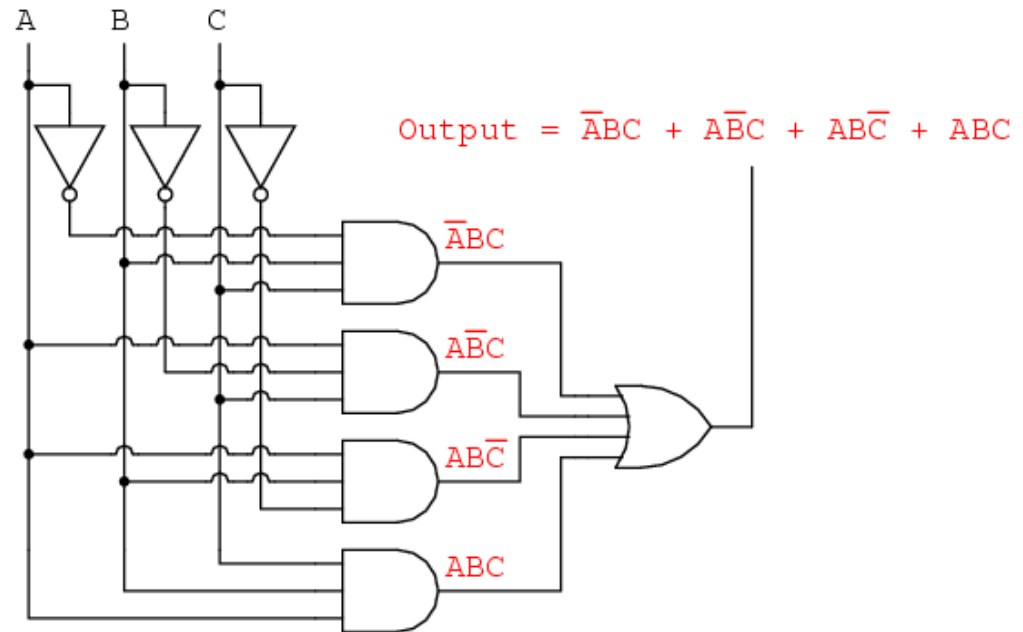
$$\text{Output} = \bar{A}BC + A\bar{B}C + AB\bar{C} + ABC$$





Finally build the circuit.

- Problem: SOP forms are often not minimal.
- Solution: Make it minimal. We'll go over two ways.

First approach: algebraic

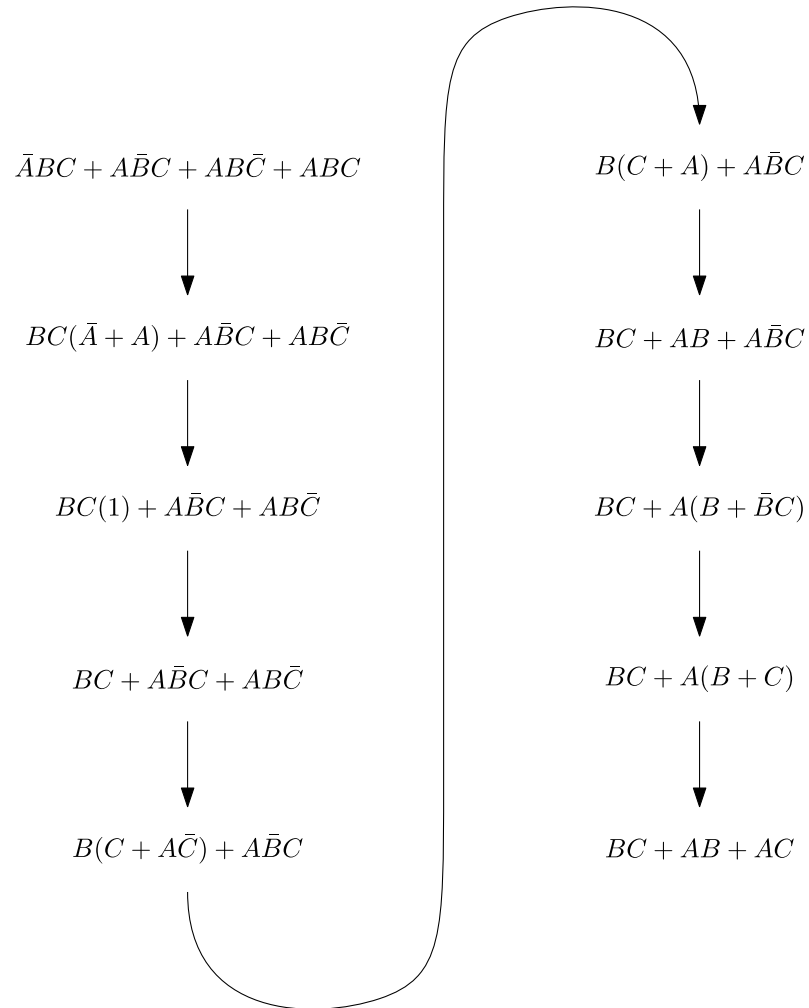

The Result

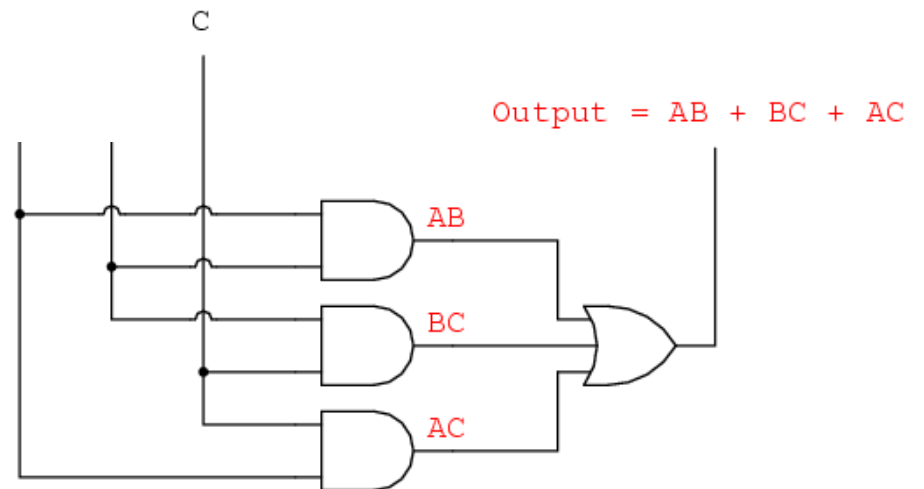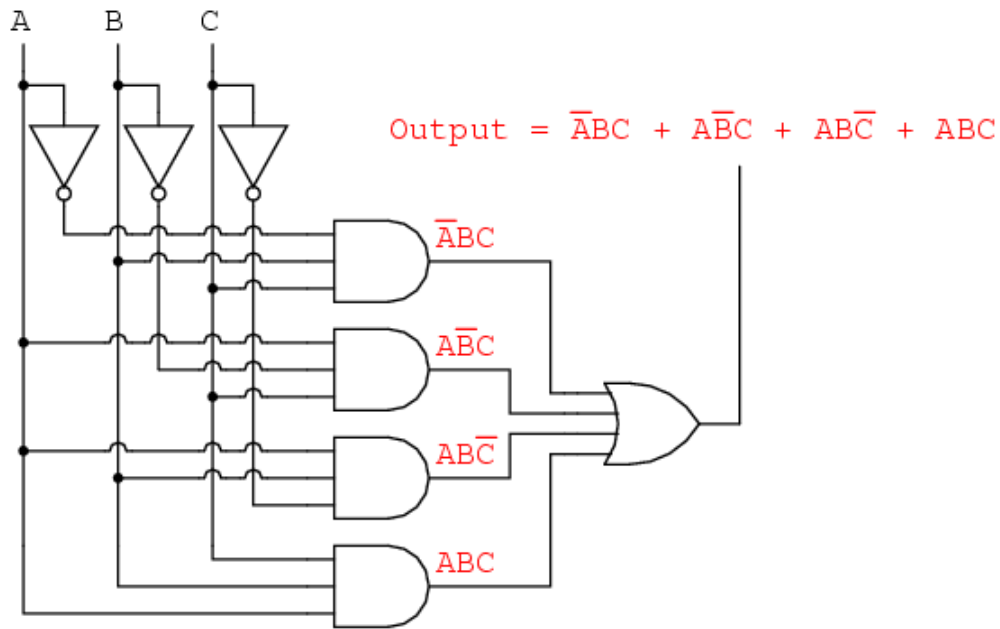




Karnaugh Maps or K-Maps

K-maps are a graphical technique to view minterms and how they relate.


The “map” is a diagram made up of squares, with each square representing a single minterm.

Minterms resulting in a “1” are marked as “1”, all others are marked “0”

2 Variable K-Map

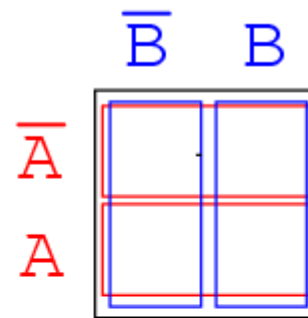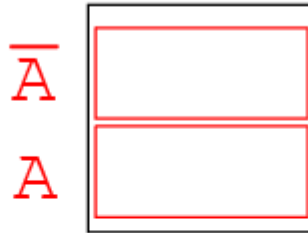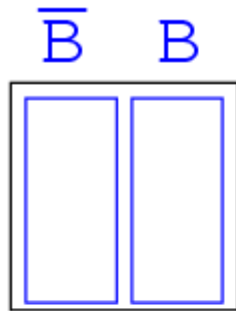


2 Variable K-Map

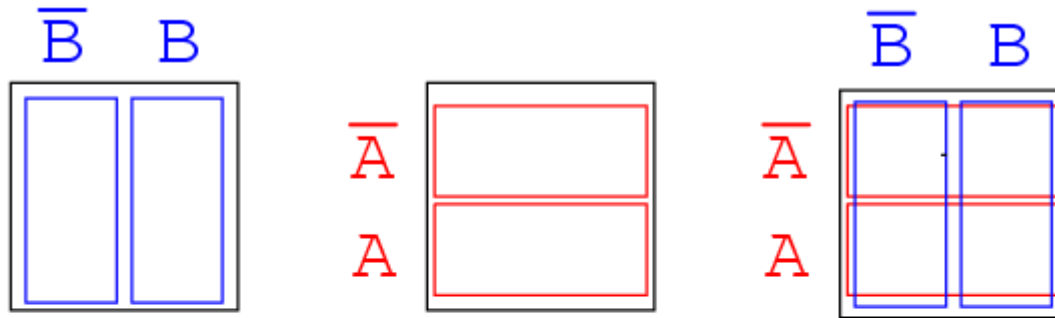

A	B	Output
0	0	0
0	1	1
1	0	0
1	1	1

A \ B	0	1
0		
1		



2 Variable K-Map

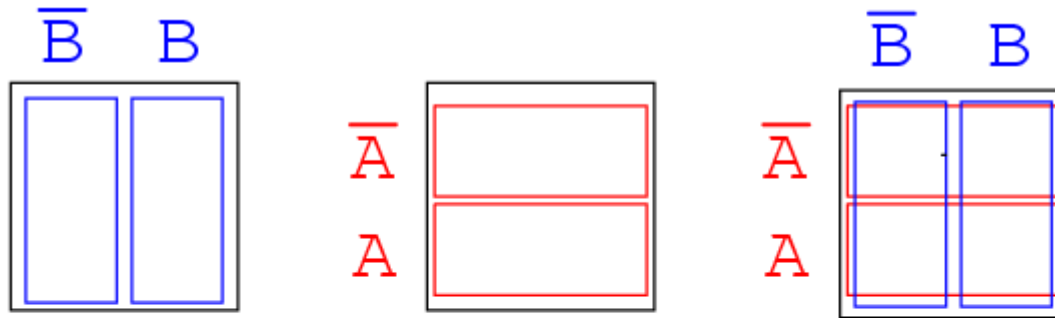


A	B	Output
0	0	0
0	1	1
1	0	0
1	1	1

A \ B	0	1
0	0	1
1	0	1

Finding Commonality

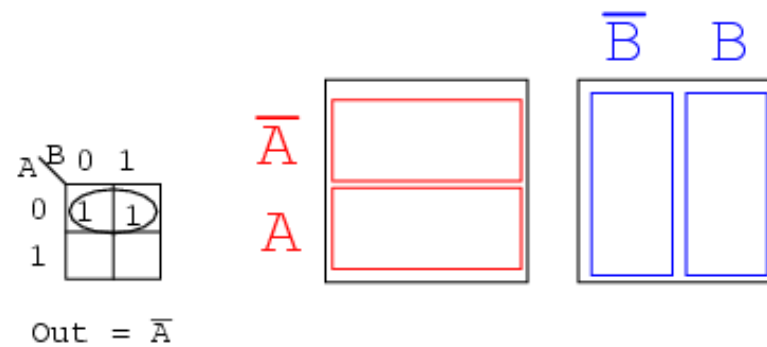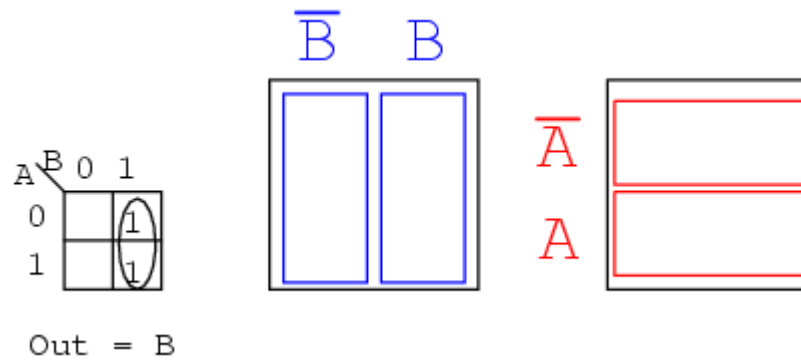


Finding the “best” solution

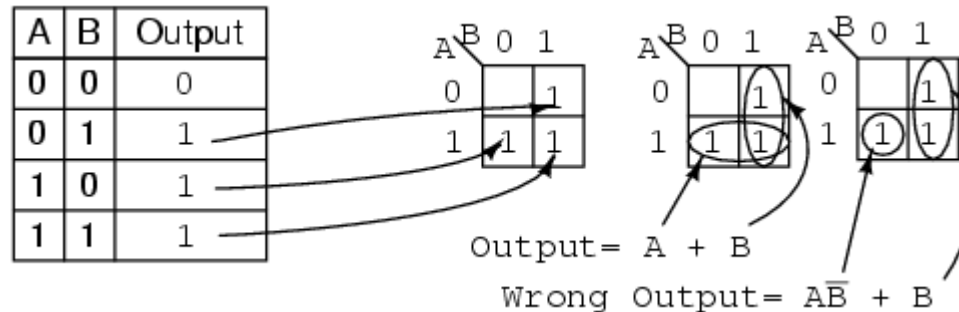



Grouping become simplified products.

Both are “correct”. “ $A+B$ ” is preferred.


Simplify Example

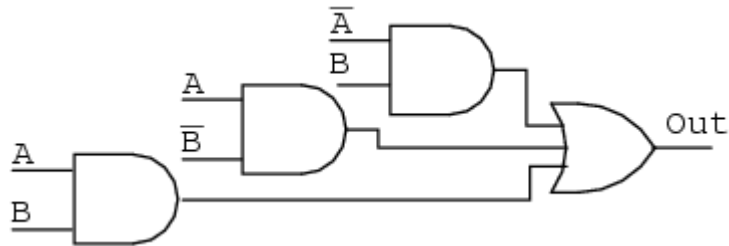

Simplify Example

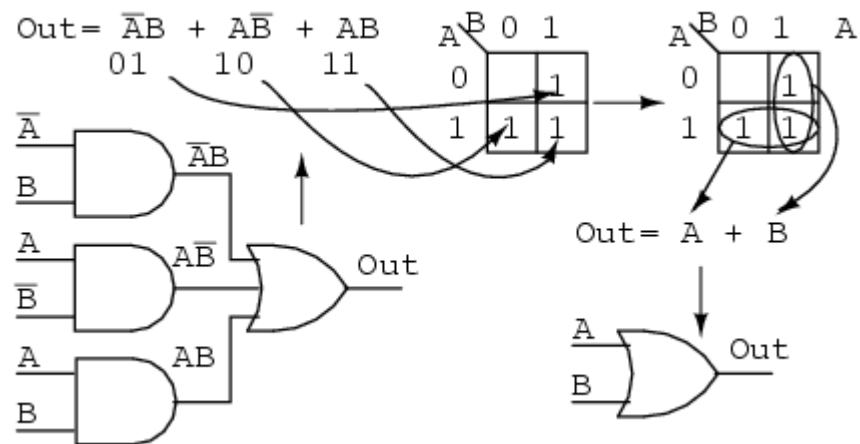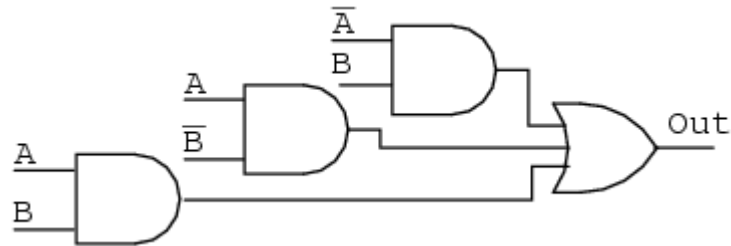

3 Variable K-Maps

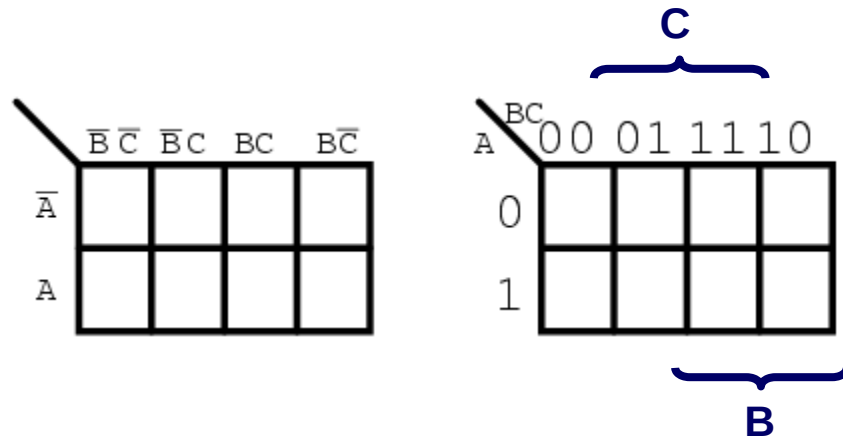

- Note in higher maps, several variables occupy a given axis
- The sequence of 1s and 0s follow a **Gray Code Sequence**.

3 Variable K-Maps

	$\overline{B}\overline{C}$	$\overline{B}C$	BC	$B\overline{C}$
\overline{A}				
A				


	$\overline{B}\overline{C}$	$\overline{B}C$	BC	$B\overline{C}$
\overline{A}				
A				

$$\text{Out} = \overline{A}\overline{B}\overline{C} + \overline{A}\overline{B}C$$


	$\overline{B}\overline{C}$	$\overline{B}C$	BC	$B\overline{C}$
\overline{A}	1	1		
A				

$$\text{Out} = \overline{A}\overline{B}$$

3 Variable K-Maps

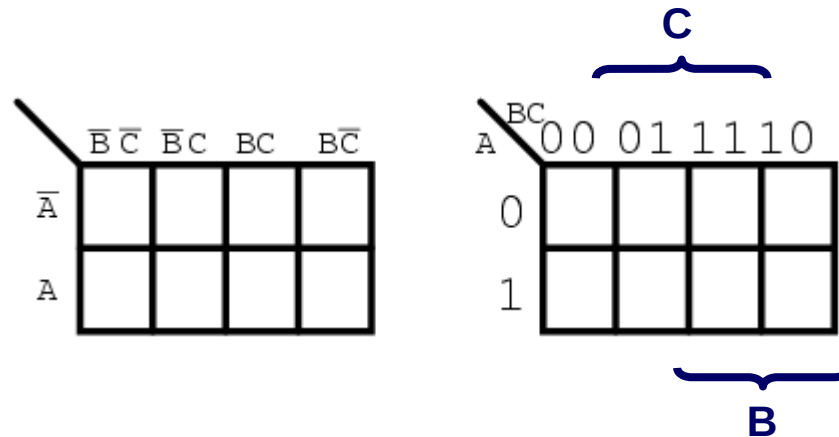

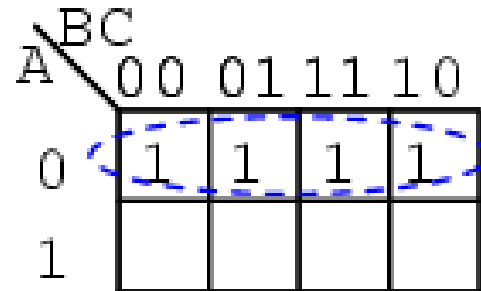
$$\text{Out} = \overline{A}\overline{B}\overline{C} + \overline{A}\overline{B}C + \overline{A}BC + \overline{A}B\overline{C}$$




$$\text{Out} = \overline{A}$$

3 Variable K-Maps

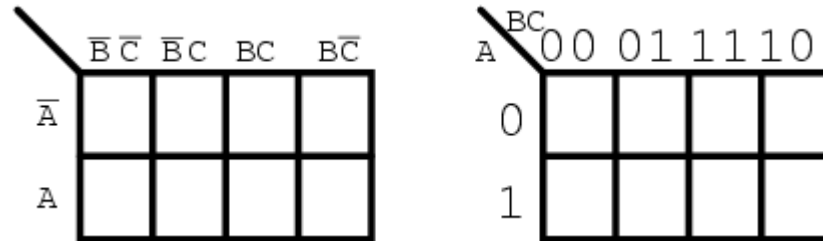

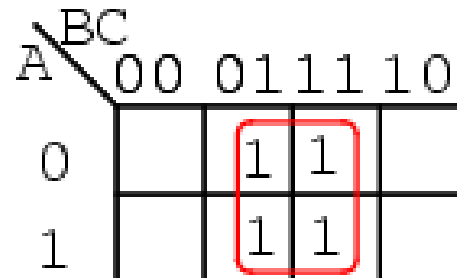
$$\text{Out} = \overline{A}\overline{B}C + \overline{A}BC + A\overline{B}C + ABC$$




$$\text{Out} = C$$

3 Variable K-Maps


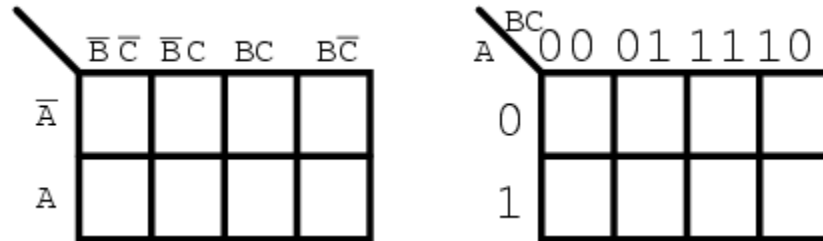

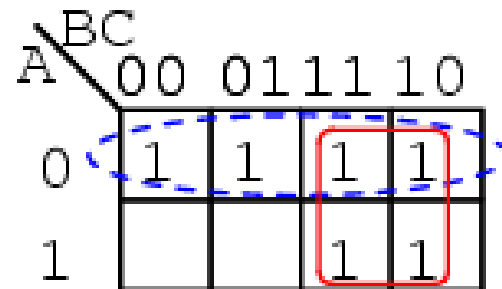
$$\text{Out} = \overline{A}\overline{B}\overline{C} + \overline{A}\overline{B}C + \overline{A}BC + \overline{A}B\overline{C} + ABC + AB\overline{C}$$




$$\text{Out} = \overline{A} + B$$


3 Variable K-Maps

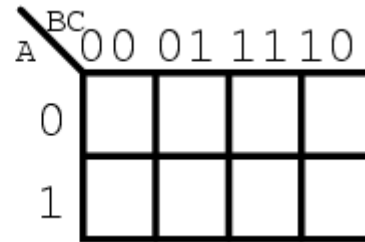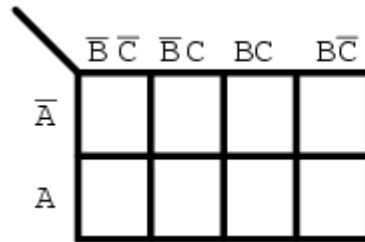

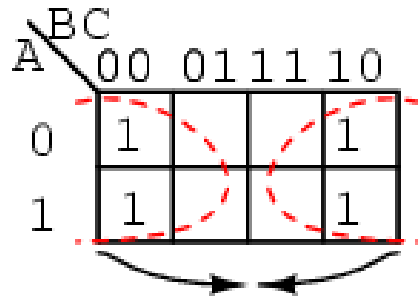
$$\text{Out} = \bar{A}\bar{B}\bar{C} + A\bar{B}\bar{C} + \bar{A}B\bar{C} + AB\bar{C}$$



$$\text{Out} = \bar{C}$$

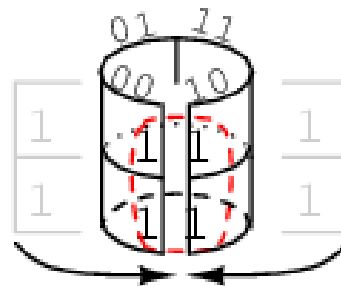

Back to our earlier example.....

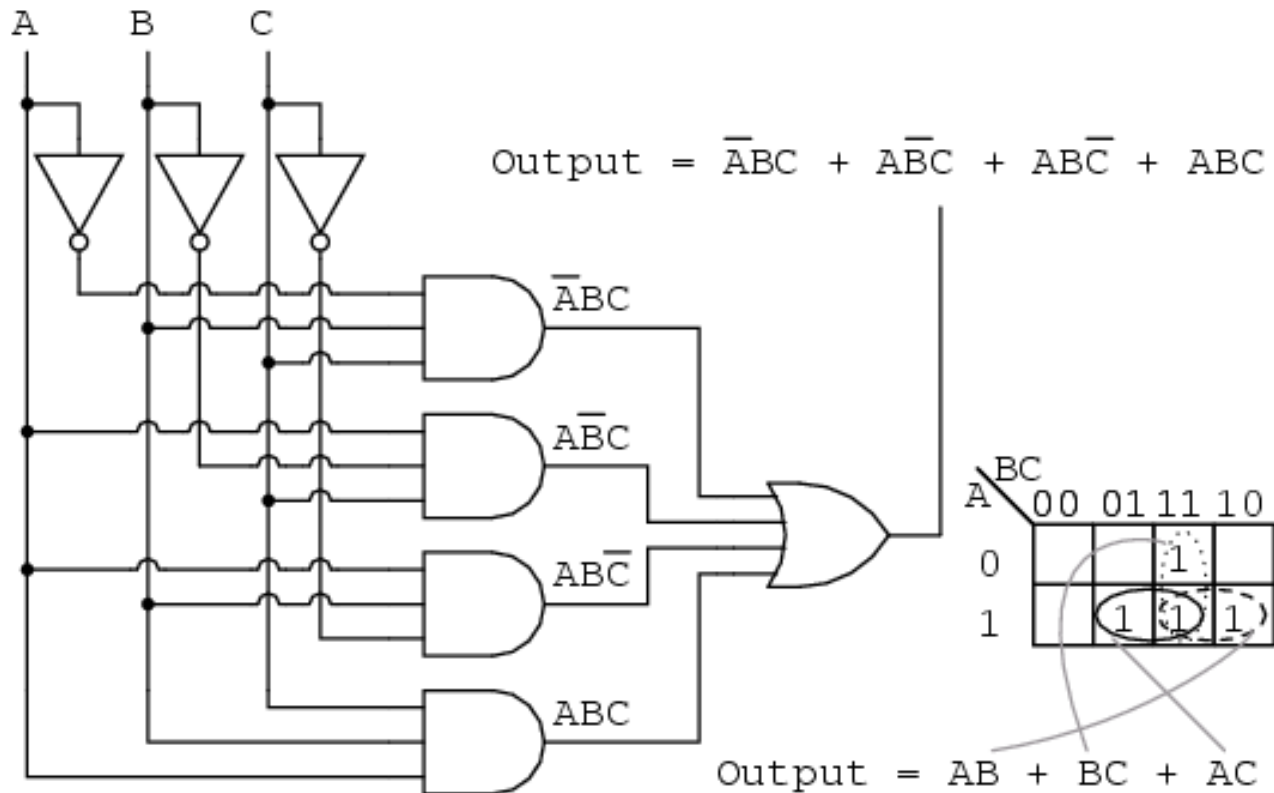

The K-map and the algebraic produce the same result.

Up... up... and let's keep going


		D			
		00	01	11	10
A	B				
	00				
	01				
	11				
	10				

C


$$\text{Out} = \overline{A}\overline{B}\overline{C}\overline{D} + \overline{A}\overline{B}C\overline{D} + A\overline{B}\overline{C}\overline{D} + A\overline{B}C\overline{D}$$

		CD			
		00	01	11	10
A	B				
	00	1			1
	01				
	11				
	10	1			1

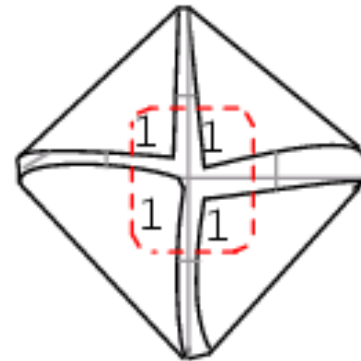
$$\text{Out} = \overline{B}\overline{D}$$



Few more examples

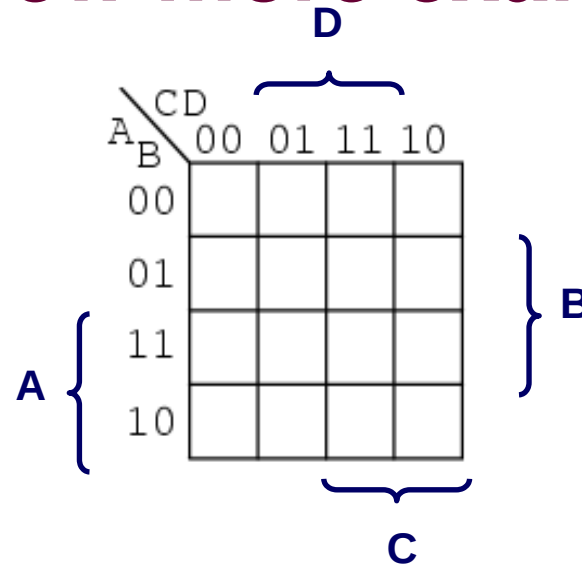
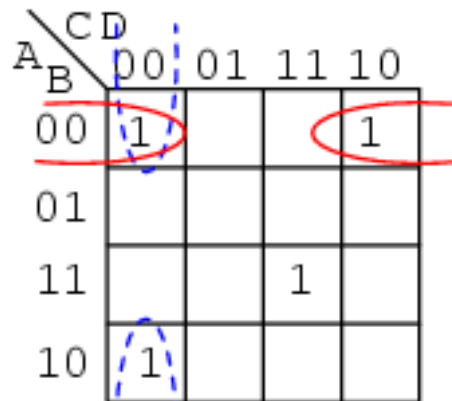
$$\text{Out} = \overline{A}\overline{B}\overline{C}\overline{D} + \overline{A}\overline{B}C\overline{D} + A\overline{B}\overline{C}\overline{D} + ABCD$$



$$\text{Out} = \overline{B}\overline{C}\overline{D} + \overline{A}\overline{B}\overline{D} + ABCD$$

Few more examples

		D			
		CD			
A	B	00	01	11	10
A	00				
	01				
	11				
	10				
		C			
					B

$$\begin{aligned} \text{Out} = & \bar{A}\bar{B}\bar{C}\bar{D} + \bar{A}\bar{B}\bar{C}D + \bar{A}\bar{B}C\bar{D} \\ & + \bar{A}B\bar{C}\bar{D} + \bar{A}B\bar{C}D + \bar{A}BC\bar{D} \\ & + AB\bar{C}\bar{D} + AB\bar{C}D + ABC\bar{D} \end{aligned}$$

		CD			
A	B	00	01	11	10
00		1	1	1	
01		1	1	1	
11		1	1	1	
10					

		CD			
A	B	00	01	11	10
00		1	1	1	
01		1	1	1	
11		1	1	1	
10					

		CD			
A	B	00	01	11	10
00		1	1	1	
01		1	1	1	
11		1	1	1	
10					

$$\text{Out} = \bar{A}\bar{C} + \bar{A}D + B\bar{C} + BD$$

Don't Care Conditions

- Let $F = AB + \overline{A}\overline{B}$
- Suppose we know that a disallowed input combo is $A=1, B=0$
- Can we replace F with a simpler function G whose output matches for all inputs we do care about?
- Let H be the function with Don't-care conditions for obsolete inputs

Inputs will not occur →

A	B	F	H	G
0	0	1	1	1
0	1	0	0	0
1	0	0	X	1
1	1	1	1	1

$$G = AB + \overline{B}$$

- Both F & G are appropriate functions for H
- G can substitute for F for valid input combinations

Don't Cares can Greatly Simplify Circuits

Sometimes “don't cares” greatly simplify circuitry

D					
	1	X	X	X	
	X	1	X	X	
	0	0	1	X	B
A	0	0	X	1	
				C	

$$\bar{A}\bar{B}\bar{C}\bar{D} + \bar{A}B\bar{C}D + ABCD + A\bar{B}C\bar{D} \text{ vs. } \bar{A} + C$$

Formal Definition of Minterms

e.g., Minterms for 3 variables A,B,C

A	B	C	minterm
0	0	0	m0 $\bar{A}\bar{B}\bar{C}$
0	0	1	m1 $\bar{A}\bar{B}C$
0	1	0	m2 $\bar{A}B\bar{C}$
0	1	1	m3 $\bar{A}BC$
1	0	0	m4 $A\bar{B}\bar{C}$
1	0	1	m5 $A\bar{B}C$
1	1	0	m6 $AB\bar{C}$
1	1	1	m7 ABC

- A product term in which all variables appear once, either complemented or uncomplemented (i.e., an entry in the truth table).
- Each minterm evaluates to 1 for exactly one variable assignment, 0 for all others.
- Denoted by mX where X corresponds to the variable assignment for which $mX = 1$.

Minterm Example

(variables appear once in each minterm)

A	B	C	F	\overline{F}	minterm
0	0	0	1	0	m0 $\overline{A}\overline{B}\overline{C}$
0	0	1	1	0	m1 $\overline{A}\overline{B}C$
0	1	0	1	0	m2 $\overline{A}B\overline{C}$
0	1	1	0	1	m3 $\overline{A}BC$
1	0	0	1	0	m4 $A\overline{B}\overline{C}$
1	0	1	1	0	m5 $A\overline{B}C$
1	1	0	0	1	m6 $AB\overline{C}$
1	1	1	0	1	m7 ABC

$$\begin{aligned}
 F &= \overline{A}\overline{B}\overline{C} + \overline{A}\overline{B}C + \overline{A}B\overline{C} + A\overline{B}\overline{C} + A\overline{B}C \\
 &= m0 + m1 + m2 + m4 + m5 \\
 &= \sum m(0,1,2,4,5)
 \end{aligned}$$

$$\begin{aligned}
 \overline{F} &= \overline{A}BC + AB\overline{C} + ABC \\
 &= m3 + m6 + m7 \\
 &= \sum m(3,6,7)
 \end{aligned}$$

Minterm Example

Circuits may be specified in the form $\sum m(0, 2, 4, 5, 6, 7, 13, 15)$, where the indices correspond to positions in a Karnaugh map:

		CD			
		00	01	11	10
AB	00	0	1	3	2
	01	4	5	7	6
	11	12	13	15	14
	10	8	9	11	10

Minterm Example

Circuits may be specified in the form $\sum m(0, 2, 4, 5, 6, 7, 13, 15)$, where the indices correspond to positions in a Karnaugh map:

		CD			
		00	01	11	10
AB	00	1	0	0	1
	01	1	1	1	1
	11	0	1	1	0
	10	0	0	0	0

Formal Definition of Maxterms

A	B	C	maxterm
0	0	0	M0 $A+B+C$
0	0	1	M1 $A+B+\bar{C}$
0	1	0	M2 $A+\bar{B}+C$
0	1	1	M3 $A+\bar{B}+\bar{C}$
1	0	0	M4 $\bar{A}+B+C$
1	0	1	M5 $\bar{A}+B+\bar{C}$
1	1	0	M6 $\bar{A}+\bar{B}+C$
1	1	1	M7 $\bar{A}+\bar{B}+\bar{C}$

- A sum term in which all variables appear once, either complemented or uncomplemented.
- Each maxterm evaluates to 0 for exactly one variable assignment, 1 for all others.
- Denoted by MX where X corresponds to the variable assignment for which $MX = 0$.

Maxterm Example

A	B	C	maxterm	F
0	0	0	M0 $A+B+C$	1
0	0	1	M1 $A+B+\bar{C}$	1
0	1	0	M2 $A+\bar{B}+C$	1
0	1	1	M3 $A+\bar{B}+\bar{C}$	0
1	0	0	M4 $\bar{A}+B+C$	1
1	0	1	M5 $\bar{A}+B+\bar{C}$	1
1	1	0	M6 $\bar{A}+\bar{B}+C$	0
1	1	1	M7 $\bar{A}+\bar{B}+\bar{C}$	0

$$\begin{aligned}
 F &= (A+\bar{B}+\bar{C}) (\bar{A}+\bar{B}+C) (\bar{A}+\bar{B}+\bar{C}) \\
 &= (M3) (M6) (M7) \\
 &= \prod M(3,6,7)
 \end{aligned}$$

Maxterm Example

Then we can find the usual sum of products:

CD

		00	01	11	10
AB	00	1	0	0	1
	01	1	1	1	1
	11	0	1	1	0
	10	0	0	0	0

$$F = BD + \bar{A}\bar{D}$$

Maxterm Example

Or the product of sums:


CD

		00	01	11	10
AB	00	1	0	0	1
	01	1	1	1	1
	11	0	1	1	0
	10	0	0	0	0

$$F = (\bar{A} + D)(B + \bar{D})$$

Converting Between Canonical Forms

	F	\overline{F}
Minterms (SOP)	$\sum m(F = 1)$	$\sum m(F = 0)$
Maxterms (POS)	$\prod M(F = 0)$	$\prod M(F = 1)$

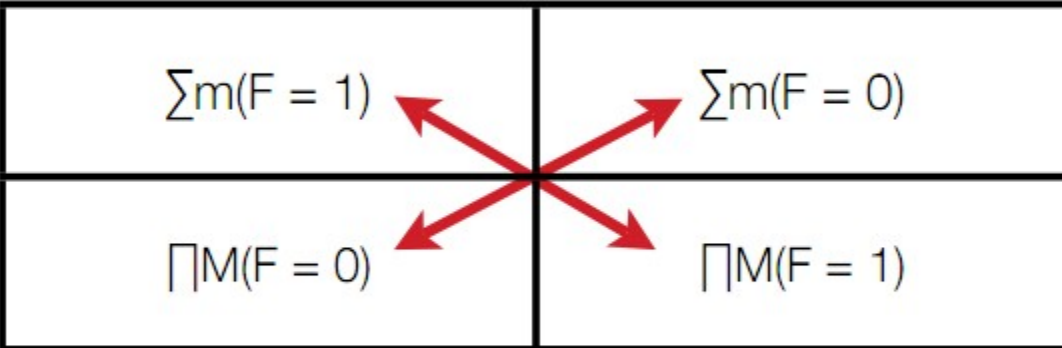

DeMorgans: same terms

Product of Sums Example

		Y Z			
		0 0	0 1	1 1	1 0
W X	0 0	1	1	0	1
	0 1	1	0	0	0
	1 1	1	0	0	0
	1 0	1	1	0	1



$$\bar{F} = YZ + XZ + YX$$

DeMorgan's

$$F = (\bar{Y} + \bar{Z})(\bar{Z} + \bar{X})(\bar{Y} + \bar{X})$$


K-maps and Implicants

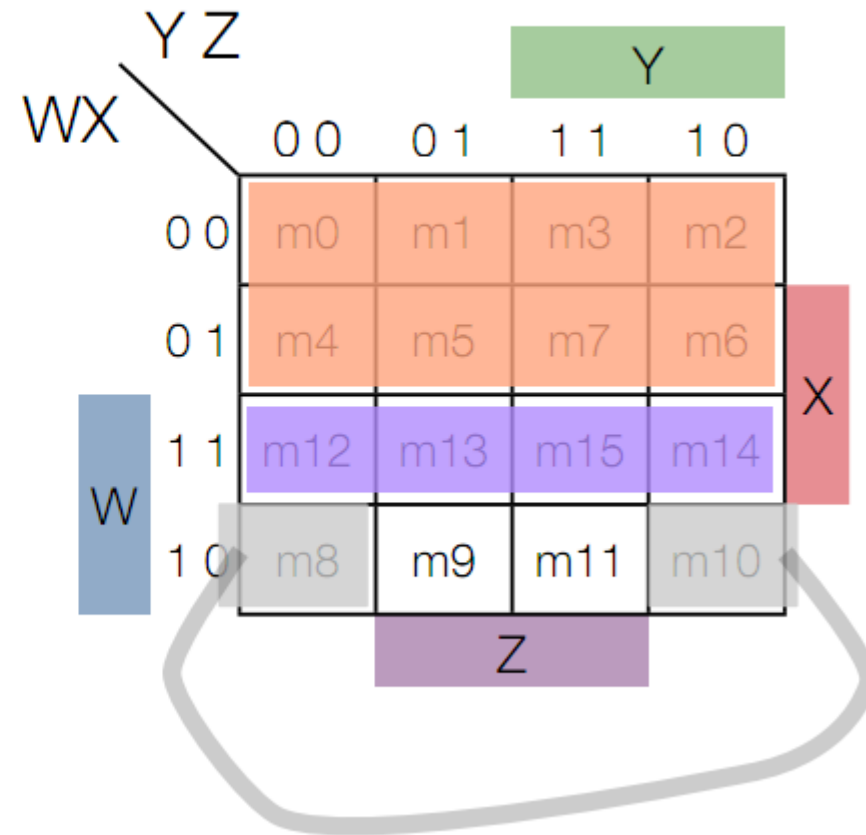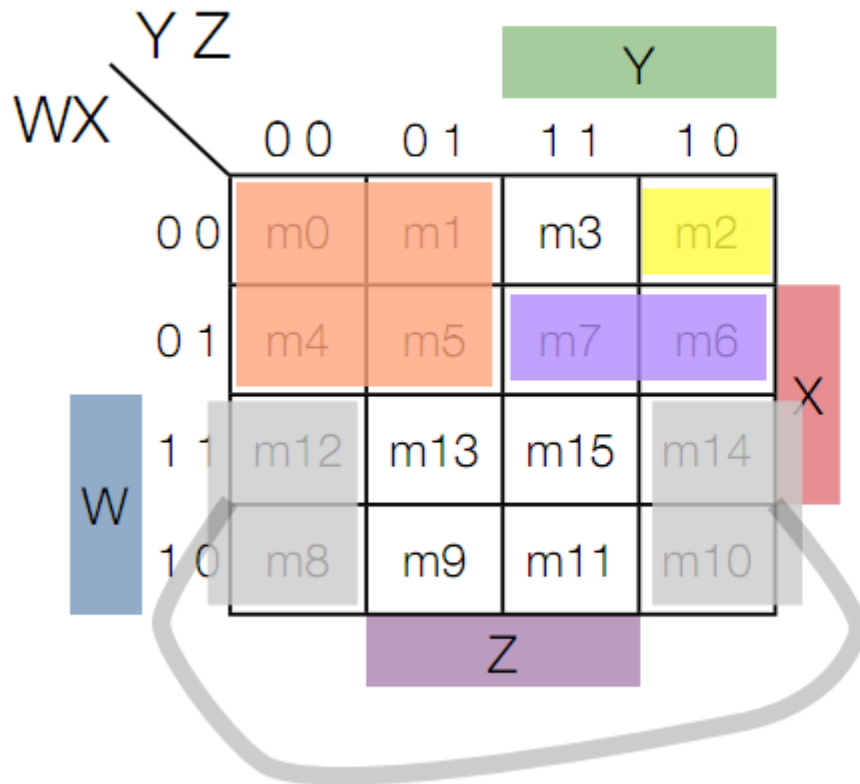- **Implicant:** a product term, which, viewed in a K-Map is a $2^i \times 2^j$ size “rectangle” (possibly wrapping around) where $i=0,1,2$, $j=0,1,2$



Implicants

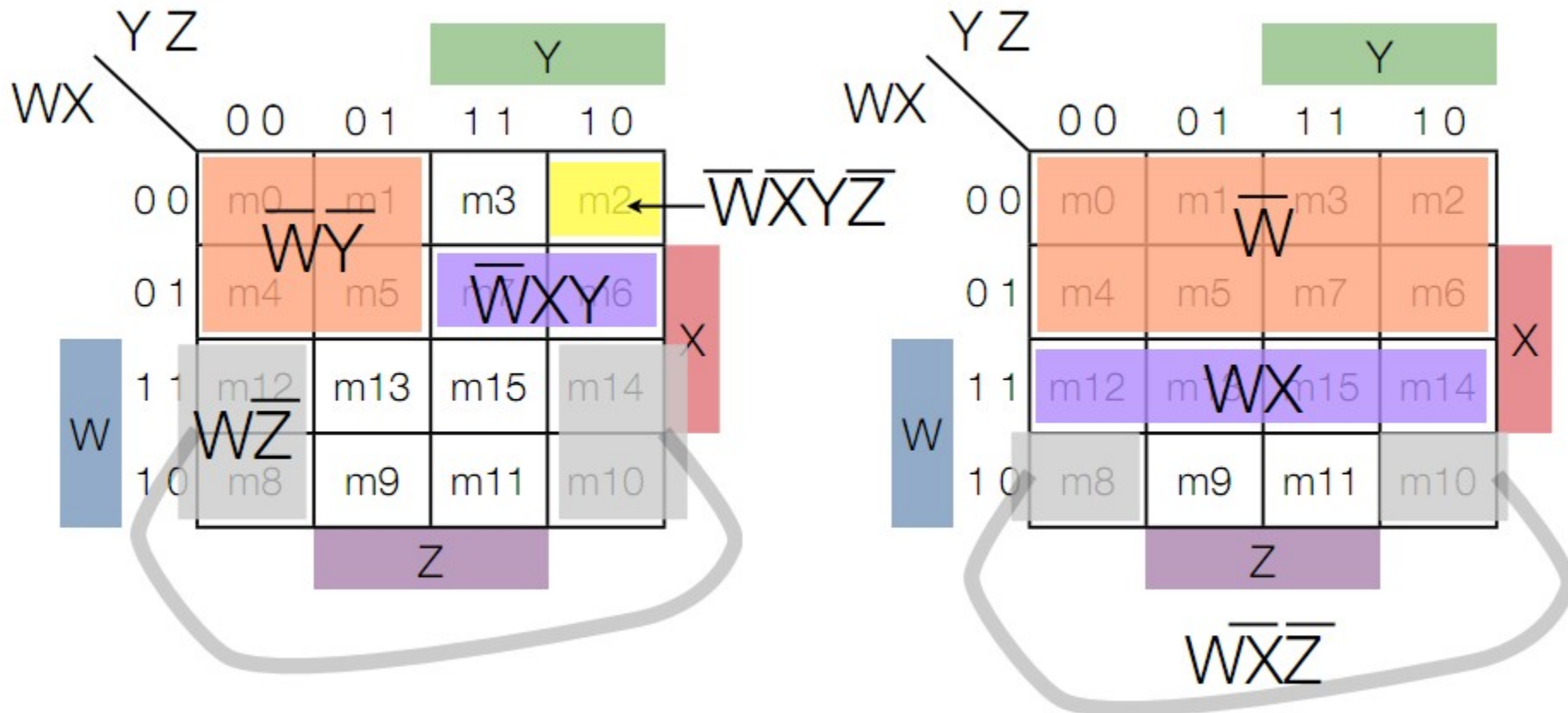- **Implicant:** a product term, which, viewed in a K-Map is a $2^i \times 2^j$ size “rectangle” (possibly wrapping around) where $i=0,1,2$, $j=0,1,2$



Note: bigger rectangles = fewer literals

More Implicant Terminology

Implicant: product term, which when viewed in a K-map, is a rectangle of 1s

Prime implicant: an implicant not contained in another implicant

Essential prime implicant: a prime implicant that is the only prime implicant to cover some minterm

Example

- List all of the prime implicants for this function
- Is any of them an essential prime implicant?
- What is a simplified expression for this function?

Karnaugh map for a 4-variable function with variables W, X, Y, and Z. The map shows prime implicants for Y, W, and Z highlighted in green, blue, and purple respectively. A red 'X' marks the cell (W=0, X=1, Y=1, Z=0).

		Y Z				
		00	01	11	10	
W X	00	0	0	1	0	
	01	1	1	1	0	X
	11	0	1	1	1	
	10	0	1	0	0	

Example

- Step 1: Identify all PIs and essential PIs
- Step 2: Include all Essential PIs in the circuit (Why?)
- Step 3: If any 1-valued minterms are uncovered by EPIs, choose PIs that are “big” and do a good job covering
- Selection Rule: a heuristic for usually choosing “good” PIs: choose the PIs that minimize overlap with one another and with EPIs

Red bounds are EPIs (solo-covered minterm shown in red)

1	1	0	0
0	1	1	1
1	1	1	1
1	1	0	0


Also need
(purple or blue) and
(yellow or green)

All blue PIs or all
green PIs cover

No EPIs!

1	1	0	0
0	1	1	0
0	0	1	1
1	0	0	1


Design Example

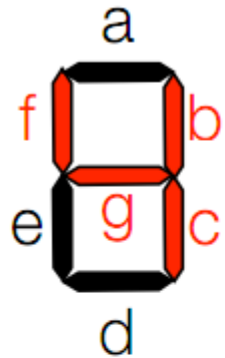


e.g., what outputs
“lights up” when input
 $V=4$?

Input					Output						
Va	W	X	Y	Z	a	b	c	d	e	f	g
0	0	0	0	0	1	1	1	1	1	1	0
1	0	0	0	1	0	1	1	0	0	0	0
2	0	0	1	0	1	1	0	1	1	0	1
3	0	0	1	1	1	1	1	1	0	0	1
4	0	1	0	0	0	1	1	0	0	1	1
5	0	1	0	1	1	0	1	1	0	1	1
6	0	1	1	0	1	0	1	1	1	1	1
7	0	1	1	1	1	1	1	0	0	0	0
8	1	0	0	0	1	1	1	1	1	1	1
9	1	0	0	1	1	1	1	0	0	1	1
X	1	0	1	0	X	X	X	X	X	X	X
X	1	0	1	1	X	X	X	X	X	X	X
X	1	1	0	0	X	X	X	X	X	X	X
X	1	1	0	1	X	X	X	X	X	X	X
X	1	1	1	0	X	X	X	X	X	X	X
X	1	1	1	1	X	X	X	X	X	X	X

Design Example

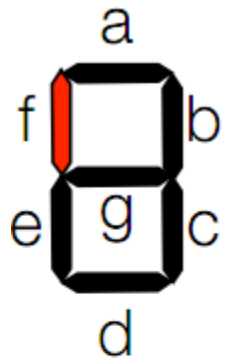


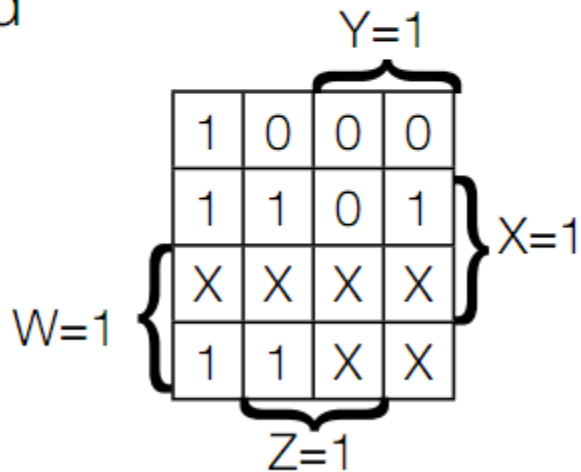For what values does output f “light up” for?



Input					Output						
Va	W	X	Y	Z	a	b	c	d	e	f	g
0	0	0	0	0	1	1	1	1	1	1	0
1	0	0	0	1	0	1	1	0	0	0	0
2	0	0	1	0	1	1	0	1	1	0	1
3	0	0	1	1	1	1	1	1	0	0	1
4	0	1	0	0	0	1	1	0	0	1	1
5	0	1	0	1	1	0	1	1	0	1	1
6	0	1	1	0	1	0	1	1	1	1	1
7	0	1	1	1	1	1	1	0	0	0	0
8	1	0	0	0	1	1	1	1	1	1	1
9	1	0	0	1	1	1	1	0	0	1	1
X	1	0	1	0	X	X	X	X	X	X	X
X	1	0	1	1	X	X	X	X	X	X	X
X	1	1	0	0	X	X	X	X	X	X	X
X	1	1	0	1	X	X	X	X	X	X	X
X	1	1	1	0	X	X	X	X	X	X	X
X	1	1	1	1	X	X	X	X	X	X	X

Design Example

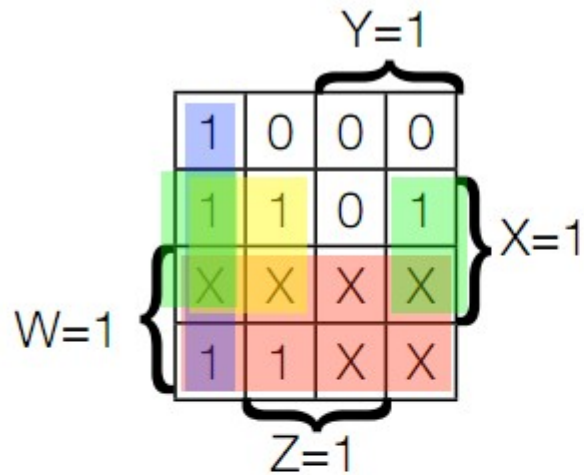

$$f = W + \bar{Y}\bar{Z} + X\bar{Z} + \bar{X}\bar{Y} = W + (X + \bar{Y})\bar{Z} + \bar{X}\bar{Y}$$

